

PUE 3141: ADVANCED DIGITAL SYSTEMS DESIGN

ASSIGNMENT 1

BY DR. MUTUGI KIRUKI

Deadline: 20th June 2022

1. Simplify the following Boolean expression:

$$Y = \overline{ACD} + B \overline{(C + A \overline{BD})} + \overline{A}B\overline{C}\overline{D}$$

2. Give the following logic expressions as a function of minterms and hence simplify using a K-map.

$$Z = A\overline{B} + \overline{A}CD + \overline{A}\overline{B}C + A\overline{B}C\overline{D}$$

3. Review the following combinational logic modules (symbols & brief description):
Multiplexer, binary decoder, magnitude comparator, Adders (full & half-adder)

4. A sequential logic circuit consists of two JK FFs as shown below. Assuming that both flip-flops are initially cleared, obtain the output signal waveforms Q_1 and Q_0 for 5 clock pulses.

